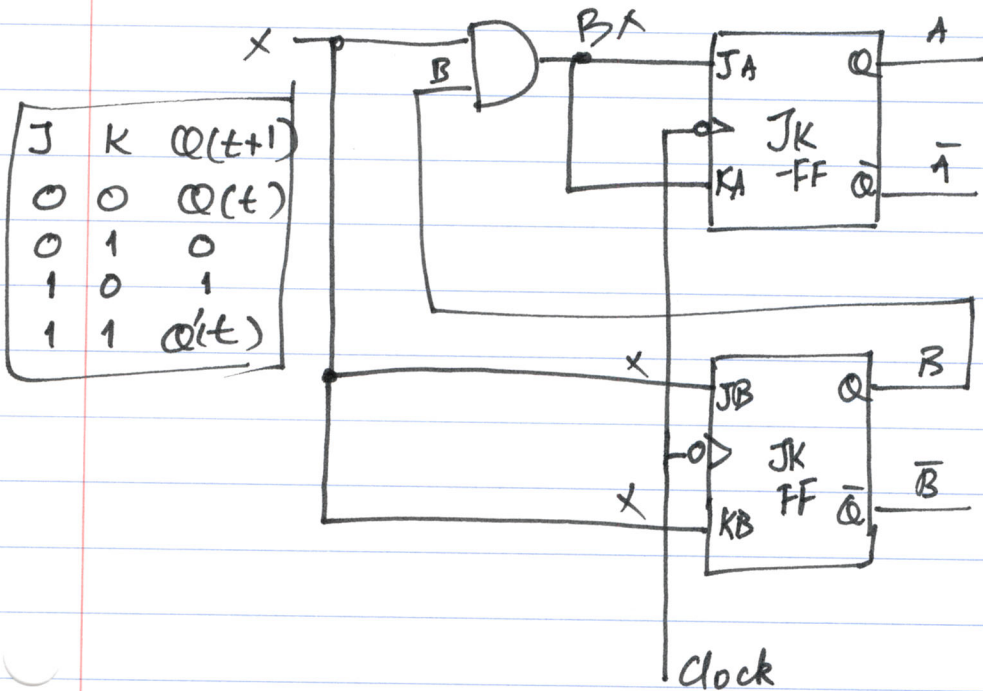


①
April 5, 2017



⇒ state diagram
word explanation

2 FF → 2 bits → 4 states

Step 1: FF - input Equation?

$J_A = Bx$ $K_A = Bx$

$J_B = x$ $K_B = x$

Step 2: state table

Current state	input	FF inputs				next state				
		A(t)	B(t)	x	J _A = Bx	K _A = Bx	J _B = x	K _B = x	A(t+1)	B(t+1)
S ₀ (0, 0)	0	0	0	0	0	0	0	0	0	0
	1	0	0	1	0	0	1	1	0	1
S ₁ (0, 1)	0	0	1	0	0	0	0	0	0	1
	1	0	1	1	1	1	1	1	1	0
S ₂ (1, 0)	0	1	0	0	0	0	0	0	1	0
	1	1	0	0	0	0	1	1	1	1
S ₃ (1, 1)	0	1	1	0	0	0	0	0	1	1
	1	1	1	1	1	1	1	1	0	0


Step 3: state diagram

April 5, 2017

(2)

2 FFs

2 bits \Rightarrow 4 states

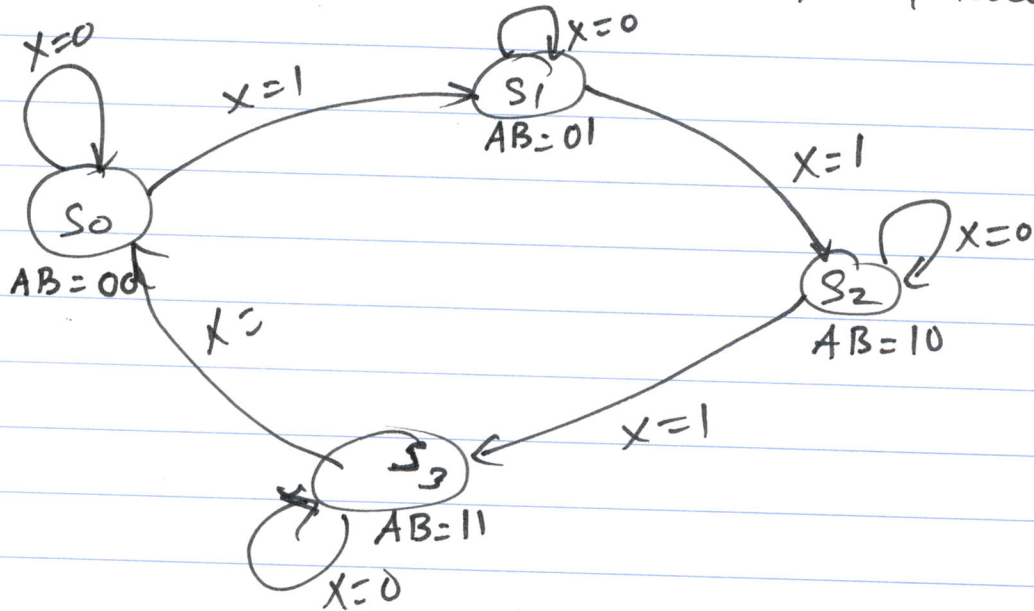

Word explanation: FSM counts its input x in fours $\{0, 1, 2, 3\}$

April 5, 2017


(3)

NAND-based decoder

74LS138

3x8 decoder

$$f(A, B, C) = \sum(4, 7)$$

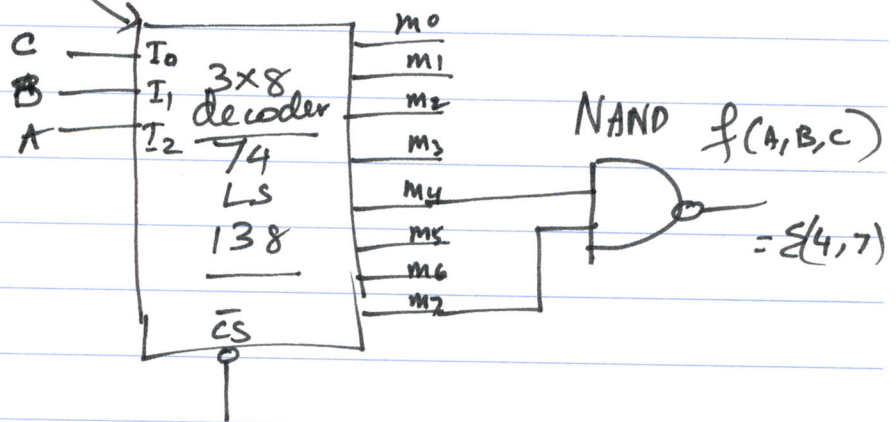

Pins +

1

2

3

on the chip 74LS138

A

B

C

External


C

B


A

your inputs

Lab 3

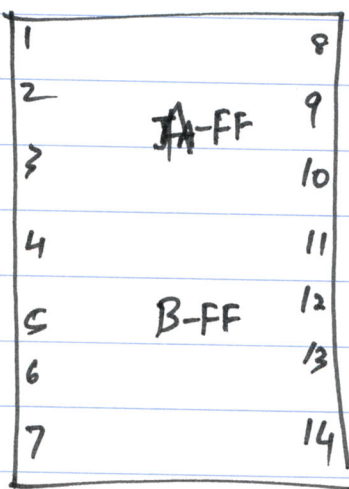

	Pin#
JA	1
KA	4
A-FF	
A	3
A ⁻	2
JB	8
KB	11
B	5
B ⁻	6
GND	7
VCC	14
clock	12, 9

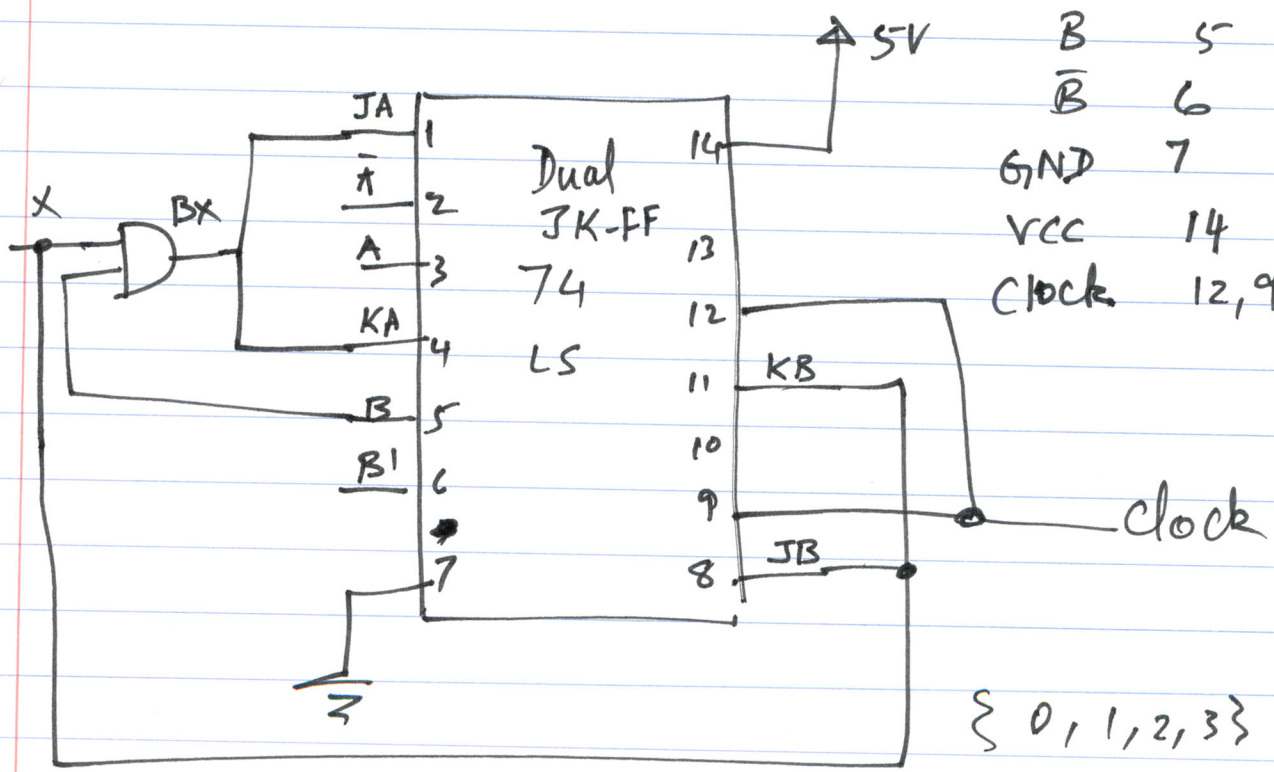

{ 0, 1, 2, 3 }