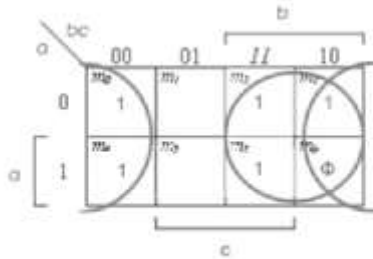



CSE 241 Digital Systems Homework 2

1. Problem 2.27 - Make a 3 variable K map for f_1 and f_2 ; minimize and implement using NAND only gates.

(a) $f_1 = b + c'$




NAND gate Only

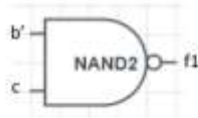


(b) $f_2' = ac' + ab + bc'$


$f_2 = (a' + c)(a' + b')(b' + c)$

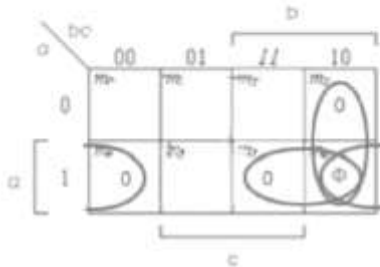


Nor gate Only

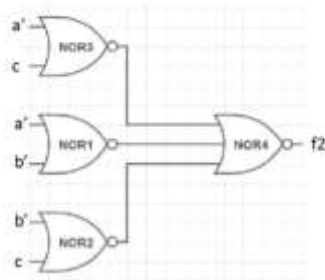


2. Problem 3.2 (d)

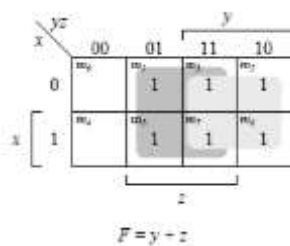

3. Problem 3.9 (d)

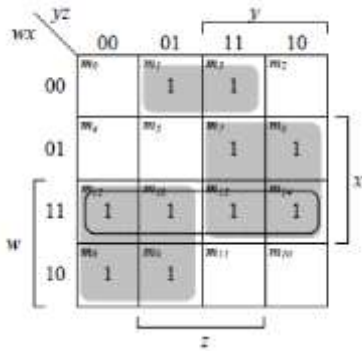

4. Problem 3.15 (d)

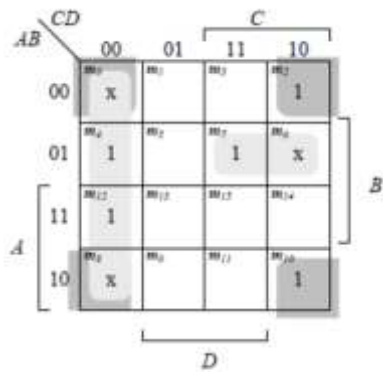




$$F = B'D' + C'D' + A'BC$$

$$F = \Sigma(0, 2, 4, 6, 7, 8, 10, 12)$$


(Ignore the second part of the question and the answer)

5. Problem 4.5

xyz	ABC
000	001
001	010
010	011
011	100
100	010
101	011
110	100
111	101

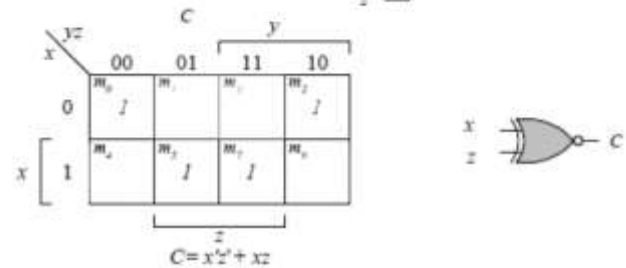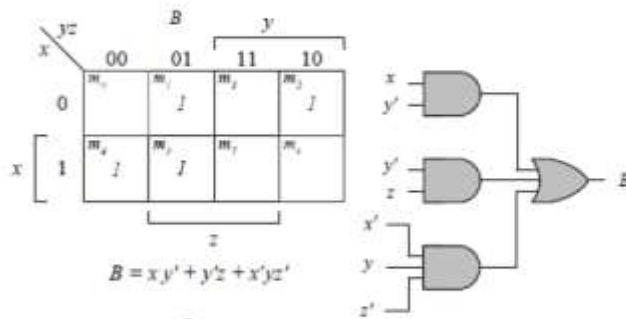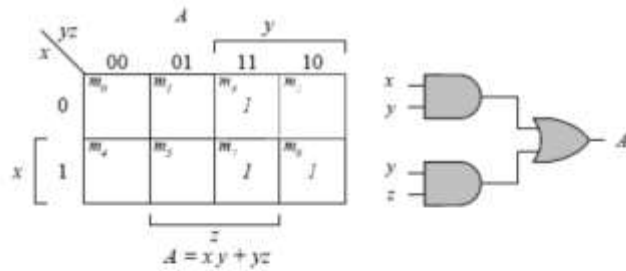


6. Problem 4.21

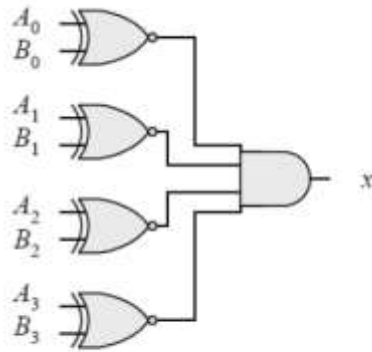

$$x = (A_0 \oplus B_0)'(A_1 \oplus B_1)'(A_2 \oplus B_2)'(A_3 \oplus B_3)'$$


7. Problem 4.26

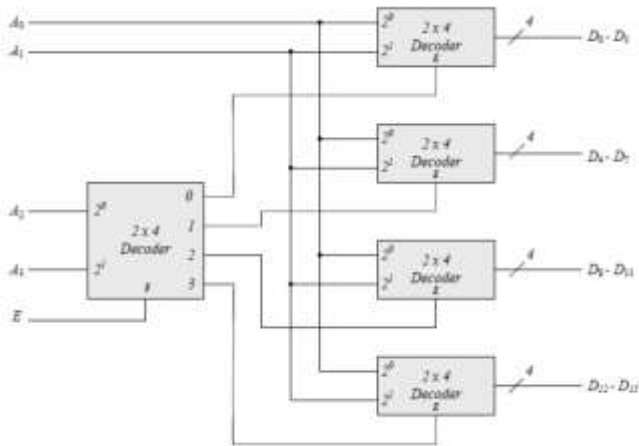

8. Problem 4.32

(a) $F = \Sigma(0, 2, 5, 8, 10, 14)$

Inputs ABCD	Max input line value	$F = \Sigma(0, 2, 5, 8, 10, 14)$
0000	0	1 $F = D'$
0001	1	0
0010	2	1 $F = D'$
0011	3	0 $F = D'$
0100	4	0 $F = D$
0101	5	1 $F = D$
0110	6	0 $F = 0$
0111	7	0 $F = 0$
1000	8	1 $F = D'$
1001	9	0 $F = D'$
1010	10	1 $F = D'$
1011	11	0 $F = D'$
1100	12	0 $F = 0$
1101	13	0 $F = 0$
1110	14	1 $F = D'$
1111	15	0 $F = D'$

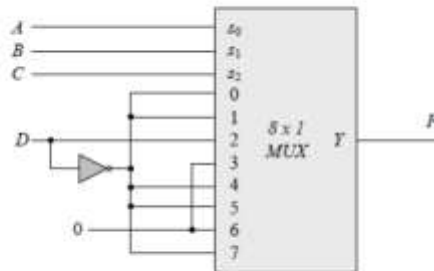

b)

$$F = \Pi(2, 6, 11) = (A' + B' + C + D')(A' + B + C + D')(A + B' + C + D)$$

$$F' = (A' + B' + C + D)' + (A' + B + C + D)' + (A + B' + C + D)'$$

$$F' = (ABC'D) + (AB'CD) + (A'BC'D) = \Sigma(13, 9, 4)$$

$$F = \Sigma(0, 1, 2, 3, 5, 6, 7, 8, 10, 11, 12, 14, 15)$$

Inputs ABCD	Max input line (ABC) Value	
000 0 0	0	$F = 1$
000 1 0	1	1
001 0 1	2	$F = 1$
001 1 1	3	$F = 1$
010 0 2	4	$F = D$
010 1 2	5	1
011 0 3	6	$F = 1$
011 1 3	7	1
100 0 4	8	$F = D'$
100 1 4	9	0
101 0 5	10	$F = 1$
101 1 5	11	1
110 0 6	12	$F = D'$
110 1 6	13	0
111 0 7	14	$F = 1$
111 1 7	15	1

