

6. The figure shows the input and output signals of a CMOS inverter. Calculate the following using the time instances mentioned in the figure.
- Fall time
 - Rise time
 - Propagation delay

