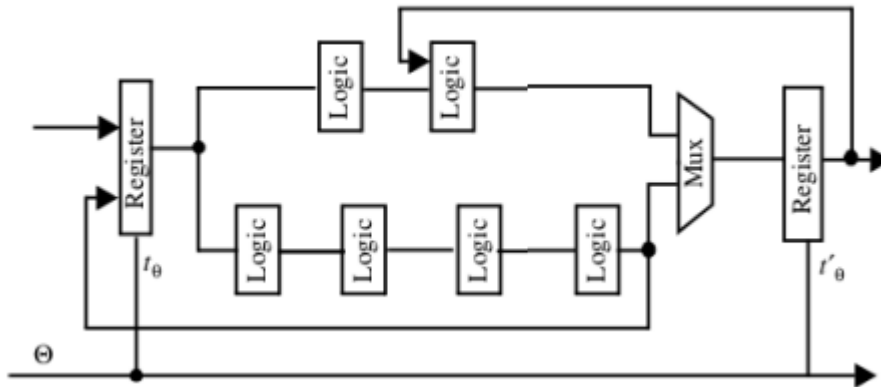



CSE 493/593 FALL 2023 HOMEWORK 5

1. Explain Clock skew and clock jitter.
2.
  - a. Explain how Dynamic Frequency Scaling can achieve low power.
  - b. Explain how Dynamic Voltage Scaling can achieve low power.
3. For the circuit shown below, assume a unit delay through the register, multiplexer and logic blocks. Assume that the registers, which are positive-edge triggered, have a unit setup time.





Determine minimum clock period disregarding clock skew.  
 (Hint:  $T \geq t_{c-q} + t_{logic} + t_{su}$ )

 4. Describe how H-tree clock distribution scheme achieves the following:
  - a. Reduced clock skew
  - b. Reduced power consumption
5. From the clock waveform given below,




- a. identify regions of (1,1) overlap and (0,0) overlap.
- b. How can you overcome this issue?  
 (Hint: From the truth table of a Full Adder, derive the SUM and CARRY equations and then design the logic)

 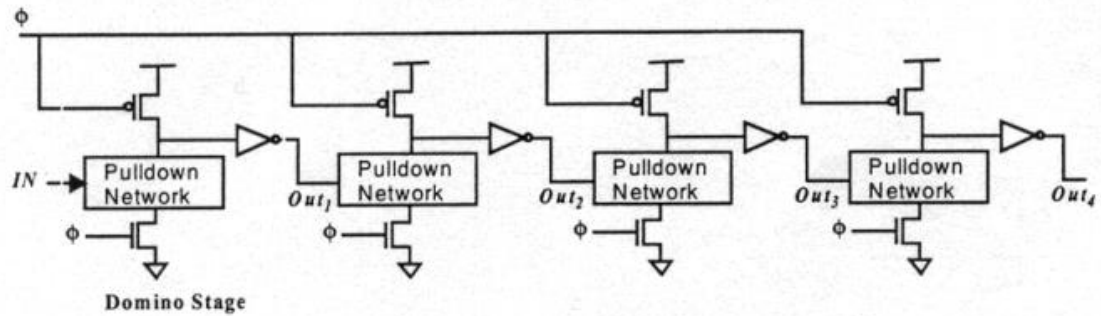6. Consider the logic function  $X = \overline{((A(B+CD)E)+(FG(H+I)))}$ . Implement the function using Dynamic CMOS Logic.
7. Consider the 4-stage domino logic circuit as shown below. Assume that each of the PDN in the figure has a single NMOS transistor. Assume the precharge time, evaluate time, propagation delay of the static inverter are all equal to  $T/2$  each (with  $T$  a time unit). Also assume zero rise and fall times for all signals. Complete the timing diagram for signals  $Out_1$ ,  $Out_2$ ,  $Out_3$  and  $Out_4$  if the  $IN$  signal goes high at the rising edge of the clock  $\phi$ . Assume clock period is  $T$ .



 8. Implement SUM and CARRY of a Full Adder in DCVSL. Assume  $A$ ,  $B$ ,  $C$  and their complements are available as inputs
9. Given a typical memory hierarchy as shown below, list them in increasing order of
  - a. Speed
  - b. Cost per unit memory
  - c. Size



10. Draw the schematic of 6T SRAM and explain how it's working.