
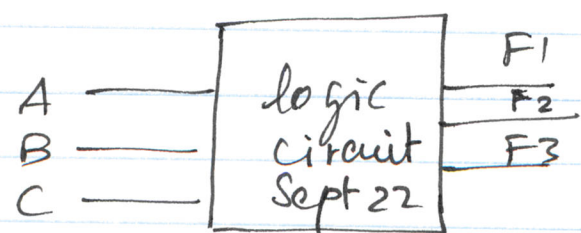
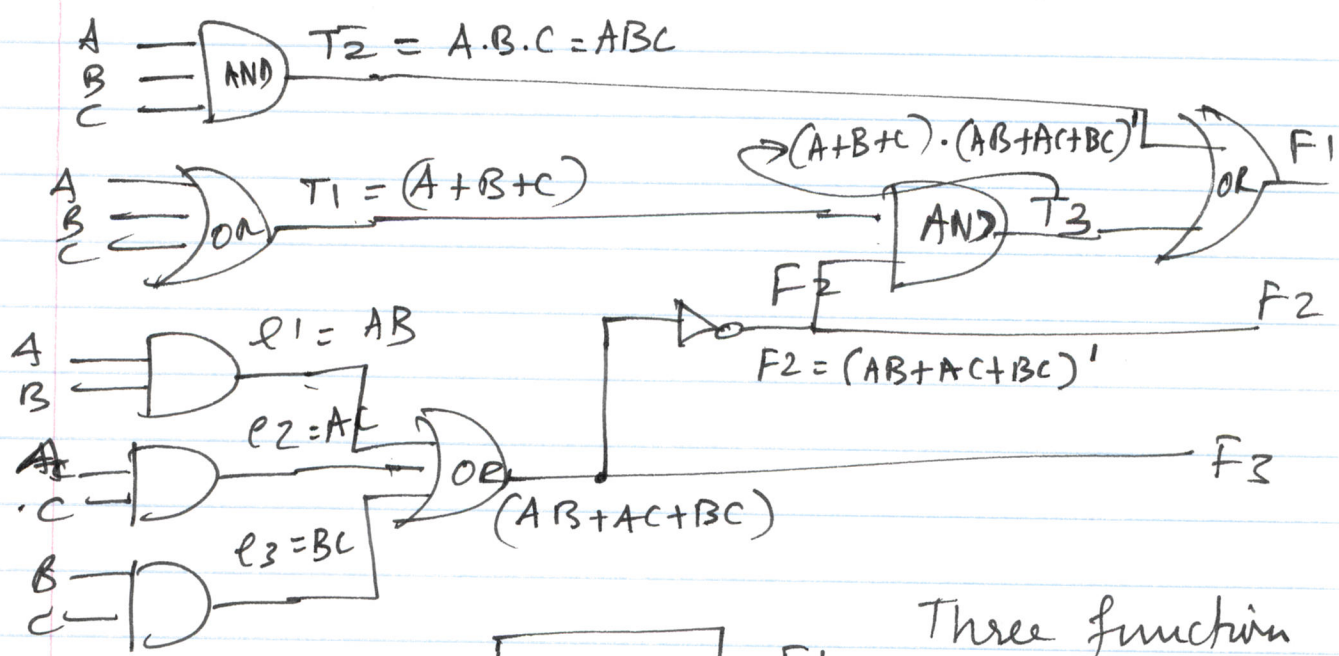


Sept 22, 2017

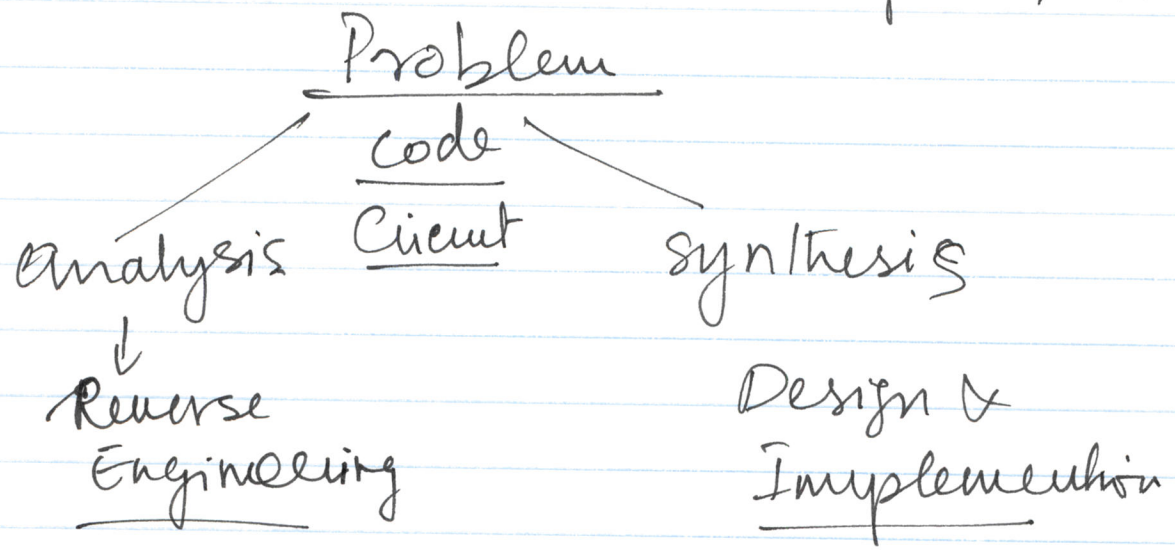


Three function
three outputs
4 inputs

$F_1(A, B, C) = (A+B+C) \cdot (AB+AC+BC)'$
 $F_2(A, B, C) = (AB+AC+BC)'$
 $F_3(A, B, C) = AB+AC+BC$

independent variables A, B, C
dependent variables F1, F2, F3

scale of integration

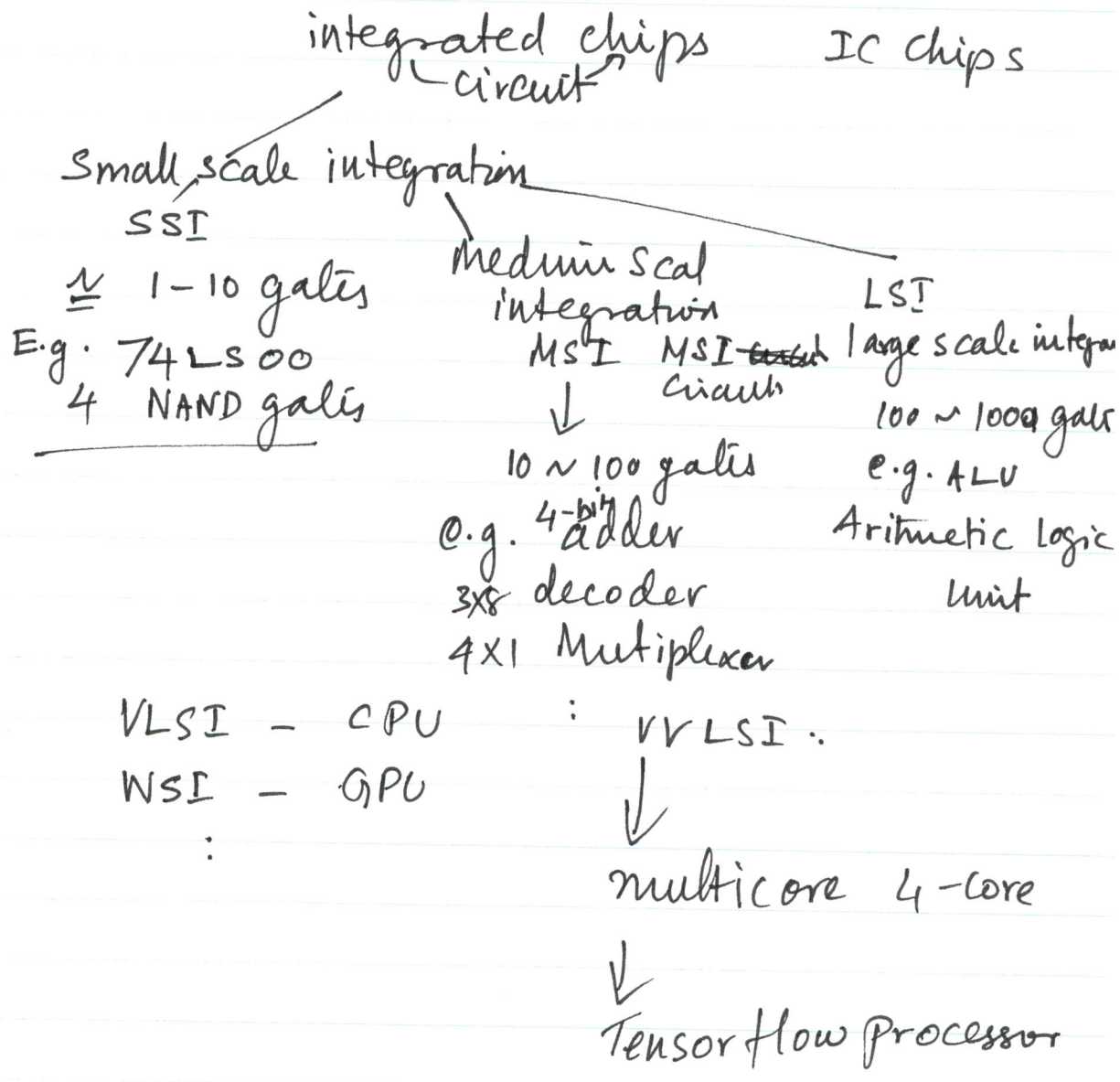


Half-adder. Design & implementation of a half-adder

2 HA - 1 FA
 many n FA n-bit adder

Sept 22, 2017

Half-adder

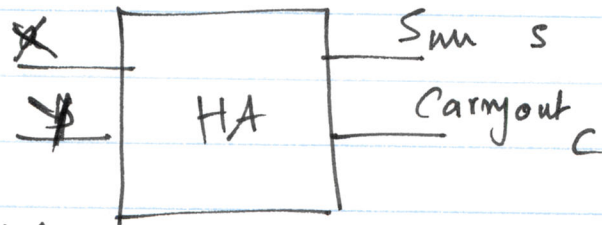

Truth Table: enumerate the operations

inputs		output	
X	Y	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1




HA 2 bit binary addition.

$$S(x,y) = x'y + xy'$$

XOR

$$C(x,y) = x \cdot y$$

AND

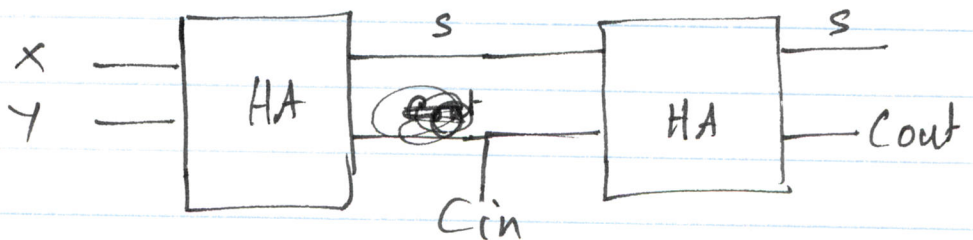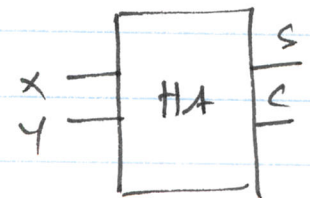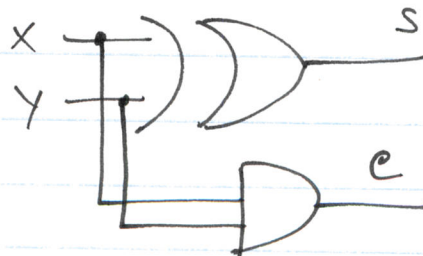

X	Y	Cin	S	Coout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Count 4
 ↑
 1

 0

K-map

$$S(x, y, C_{in}) = \sum (1, 2, 4, 7)$$

$$C(x, y, C_{in}) = \sum (3, 5, 6, 7)$$

X \ Y C _{in}	00	01	11	10
0	0	1	1	1
1	1	0	0	0

S

X \ Y C _{in}	00	01	11	10
0	0	1	1	0
1	1	1	0	0

$$C_{out} = \underline{\underline{Y C_{in} + X C_{in} + X Y}}$$

Sof minterms

$$S = \underline{\underline{X'Y'C_{in}}} + \underline{\underline{X'Y C_{in}'}} + \underline{\underline{X Y' C_{in}'}} + \underline{\underline{X Y C_{in}}}$$

$$= C_{in}'(X'Y + XY') + C_{in}(X'Y' + XY)$$


$$= C_{in}'(X \oplus Y) + C_{in}(X \oplus Y)'$$

$$= \underline{\underline{C_{in} \oplus X \oplus Y}}$$

"Rex"

$$C_{out} = \cancel{y \cdot cin} + y \cdot cin + x \cdot cin + x \cdot y$$

$$S = C_{in} \oplus x \oplus y$$

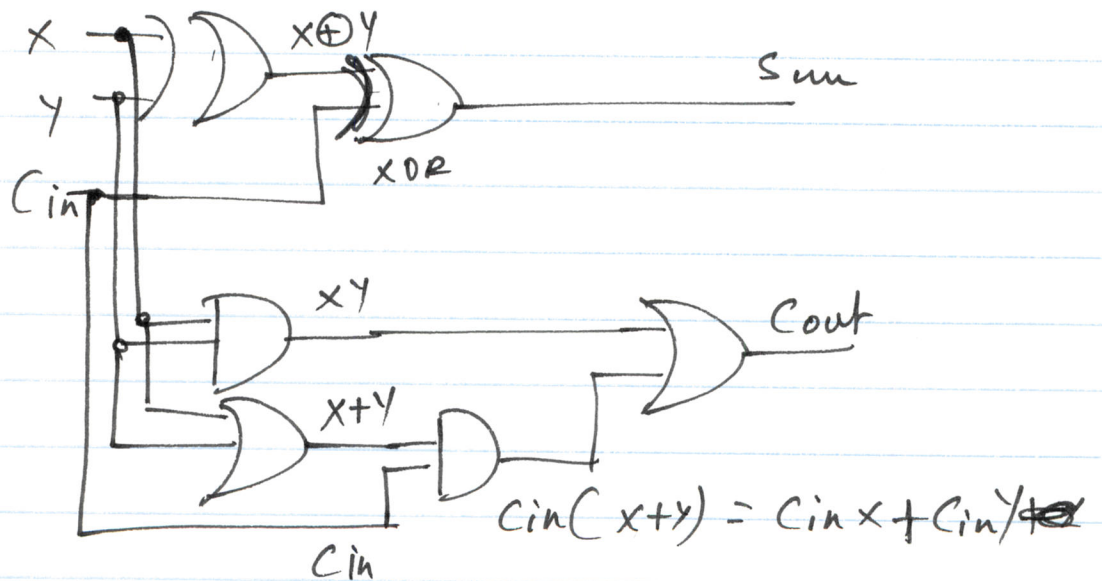

4-bit or 8 bit adder
 ↓

$4 \times 6 = 24$ galis
 4-bit FA.