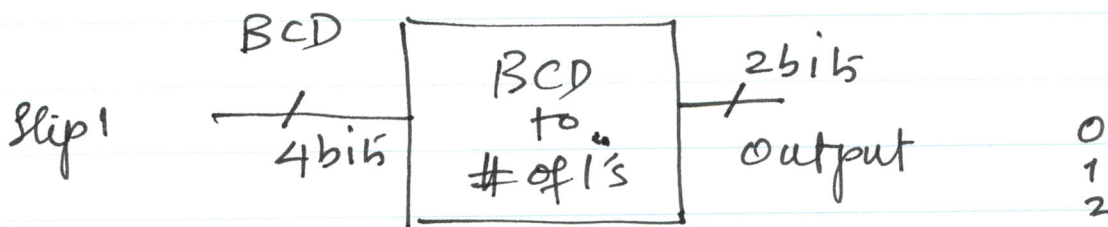


Sept 15, 2017

Problem solving using logic gates.

BCD  $\rightarrow$  odd parity

BCD  $\rightarrow$  count the number 1's in the input.



Step 2. Truth Table BCD - (0-9) inputs

BCD	A	B	C	D	$f_1$	$f_0$
0	0	0	0	0	0	0
1	0	0	0	1	0	1
2	0	0	1	0	0	1
3	0	0	1	1	1	0
4	0	1	0	0	0	1
5	0	1	0	1	1	0
6	0	1	1	0	1	0
7	0	1	1	1	1	1
8	1	0	0	0	0	1
9	1	0	0	1	1	0

?

$f_0(A, B, C, D) = ? = \{1, 2, 4, 7, 8\}$   
 $f_1(A, B, C, D) = ? = \{3, 5, 6, 7, 9\}$



Simplify the expression



Implement using gates

algebraic simplification

(2)

Sept 15, 2017

$$f_0(A, B, C, D) = \sum (m_1, m_2, m_4, m_7, m_8)$$

$$f_1(A, B, C, D) = \sum (m_3, m_5, m_6, m_7, m_9)$$

$$\rightarrow \underline{A'B'C'D} + \underline{A'B'CD'} + \cancel{A'BC'D'} + \underline{A'BC'D'} + \underline{A'BCD} + \underline{A'BC'D}$$


Sum of products:

$$f_0 = A'B'(C'D + CD) + A'B(C'D' + CD) + A'BC'D'$$

$$f_1(A, B, C, D) = \underbrace{A'B'CD}_{m_3} + \underbrace{\cancel{A'BC'D}}_{m_5} + \underbrace{A'BCD'}_{m_6} + \underbrace{A'BCD + A'BC'D}_{m_7, m_9}$$

$$= B'CD(A'+A) + \dots$$

Bus

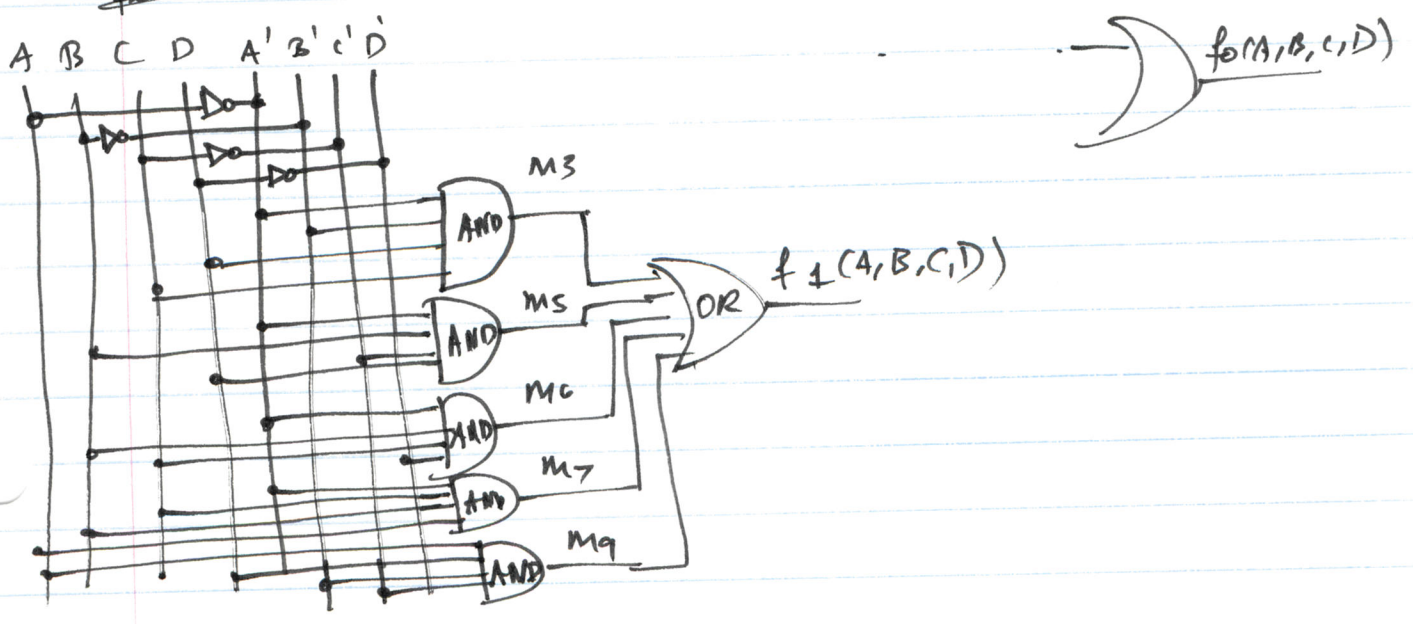

2017

Sept 15 (3)

### Improvements.

1. we can use don't care conditions in simplification

BCD      0 - 9 ↑  
 4 bits    0 - 15 ↓    6 combinations

2. Algebraic simplification

→ K-map  
 Karnaugh map

3. use only NAND gates for implementation

Problem :  $f_0(A, B, C, D) = \Sigma(1, 2, 4, 7, 8)$   
 $f_1(A, B, C, D) = \Sigma(3, 5, 6, 7, 9)$   
 $d(A, B, C, D) = \Sigma(10, 11, 12, 13, 14, 15)$   
 don't cares

never going to happen in the input.

use these if you want to, for simplification.

2-variable K-map

	B	0	1
A	0	0	1
	1	2	3

X

3-variable K-map

		BC			
		00	01	11	10
A	0	0	1	3	2
	= 0				
	= 1	4	5	7	6

# K-map

empty 4-variable map

Sept 15 (24)

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

goal:

- to group the 1's into largest groups of rectangular adjacent 1's.
- cover all 1's with min. of groups

use K-maps for simplification

f<sub>0</sub>:

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

*(Note: In the original image, the 1's in cells (0,1), (0,3), (1,1), (1,3), (3,1), (3,3), and (2,0) are circled, and a large oval encloses the 1's in the first two columns.)*

plot the fn.

- group 1: BCD
- group 2: B'C D'
- group 3: A D'
- wrap around:
- group 4: B C' D'
- group 5: A B' C' D

f<sub>1</sub>:

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

*(Note: In the original image, the 1's in cells (0,1), (0,3), (1,1), (1,3), (1,5), (1,7), (3,1), (3,3), (3,5), (3,7), and (2,0) are circled, and a large oval encloses the 1's in the first two columns.)*

- t<sub>0</sub> group 1: BC
- t<sub>1</sub> group 2: BD
- t<sub>3</sub> group 3: AD
- t<sub>11</sub> group 4: CD